



EAST WEST UNIVERSITY

Course Name : Electronic Circuits

Course Code : CSE251

Section No :06

Group No :

Experiment No : 05

Name of the Experiment : Signal Integration and Differentiation Using 741 Op-Amp

Date of allocation :

Date of submission: 6-1-2020

Submitted To : Surajit Das Barman
Senior Lecturer

Student's Name : Apurba Roy
Student's ID :2018-3-60-063

Student's Name : Monjurul Alam
Student's ID :2018-3-60-035

Objectives: 1. To study the responses of Op-Amp integrator to sinusoid and square waveforms. 2. To study the responses of Op-Amp differentiator to sinusoid and triangular waveforms.

Introduction: Operational Amplifier (Op-Amp) is a differential amplifier and can perform mathematical operations such as addition, subtraction, integration, differentiation, etc.

Circuit diagram:

integrator circuit:

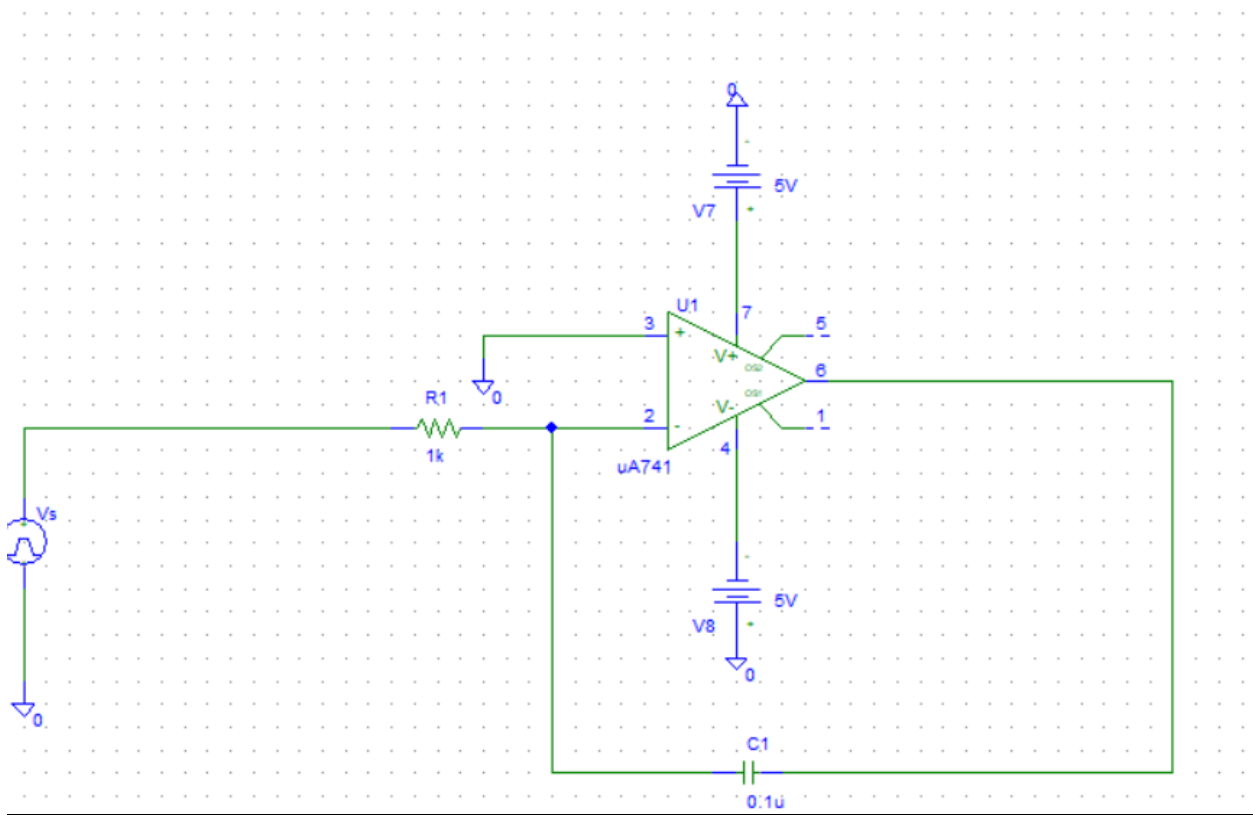


Figure 1. An Op-Amp integrator circuit

differentiator circuit:


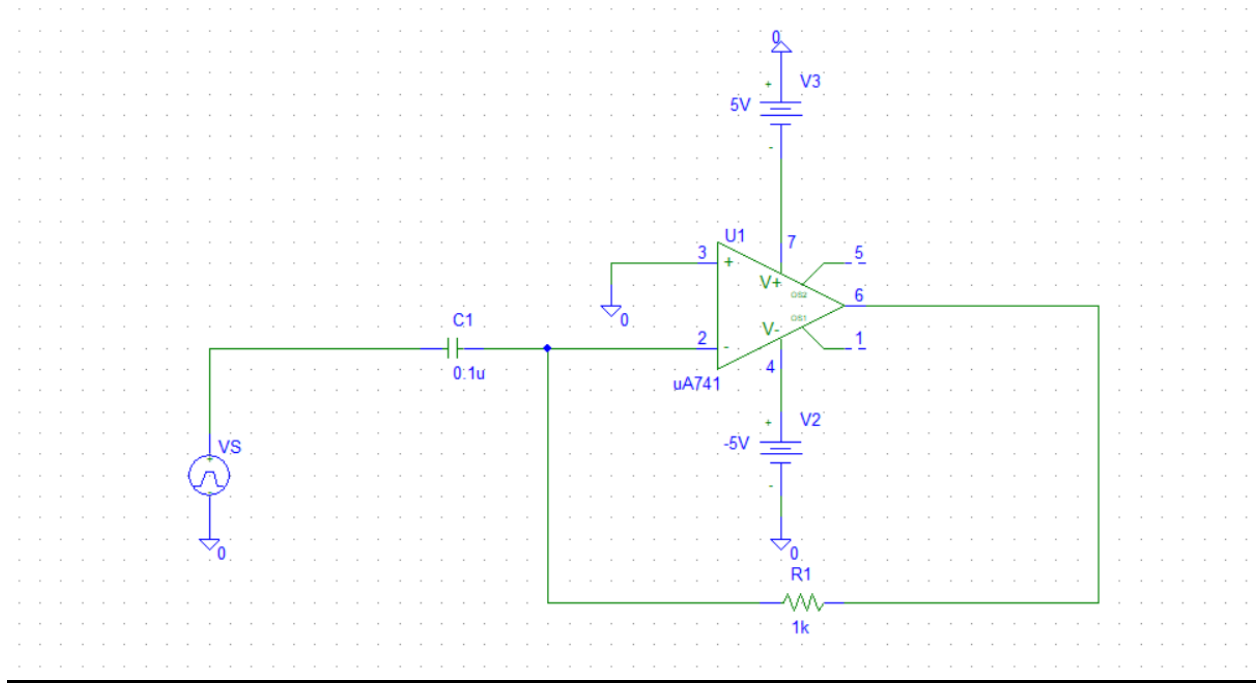
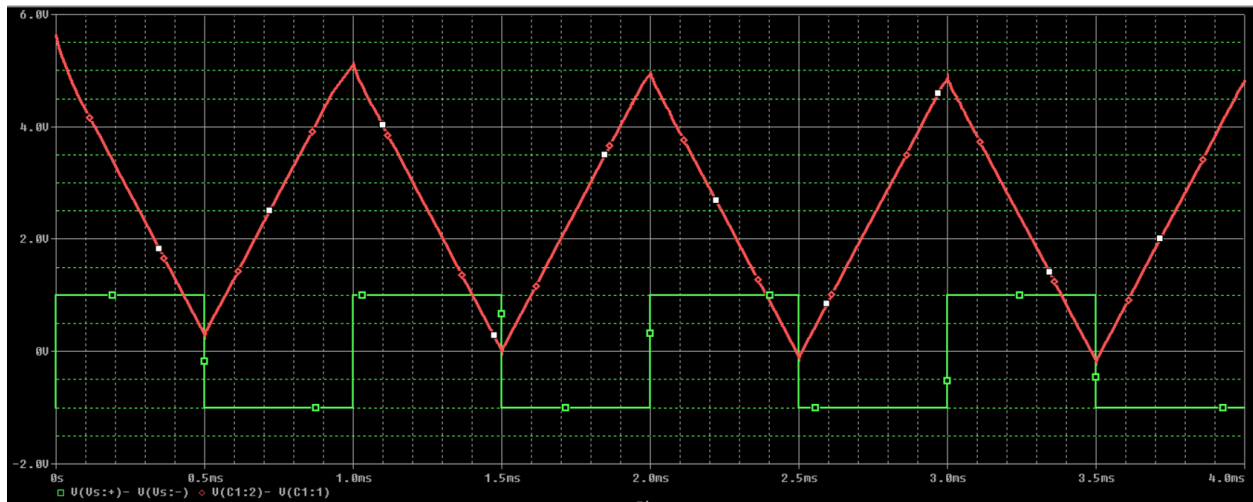


Figure 2. An Op-Amp differentiator circuit.



Post-Lab Report Questions:

Answer:

Integrator:

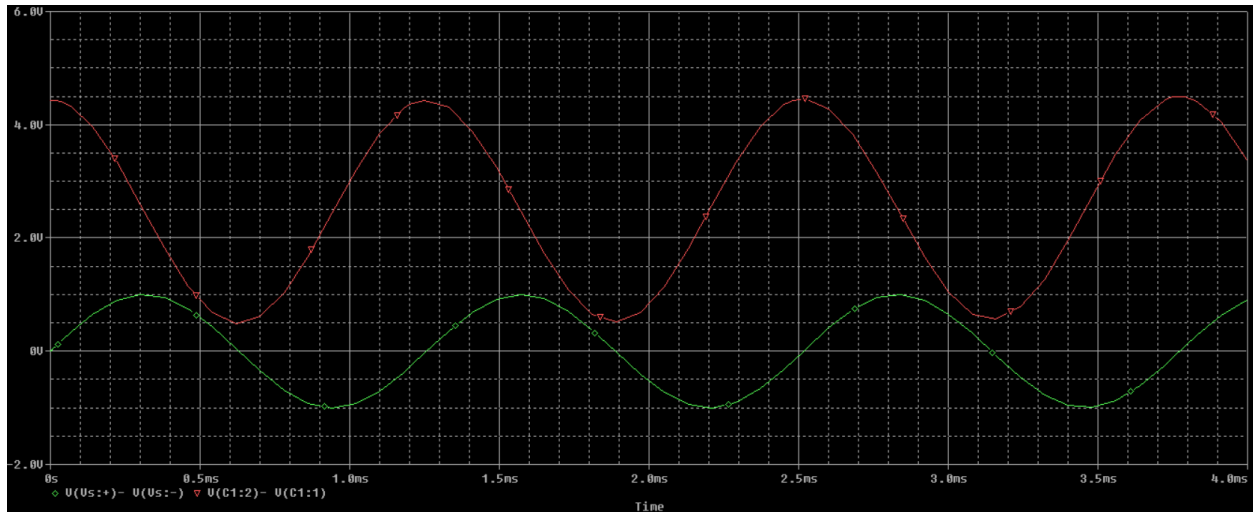

Differentiator:

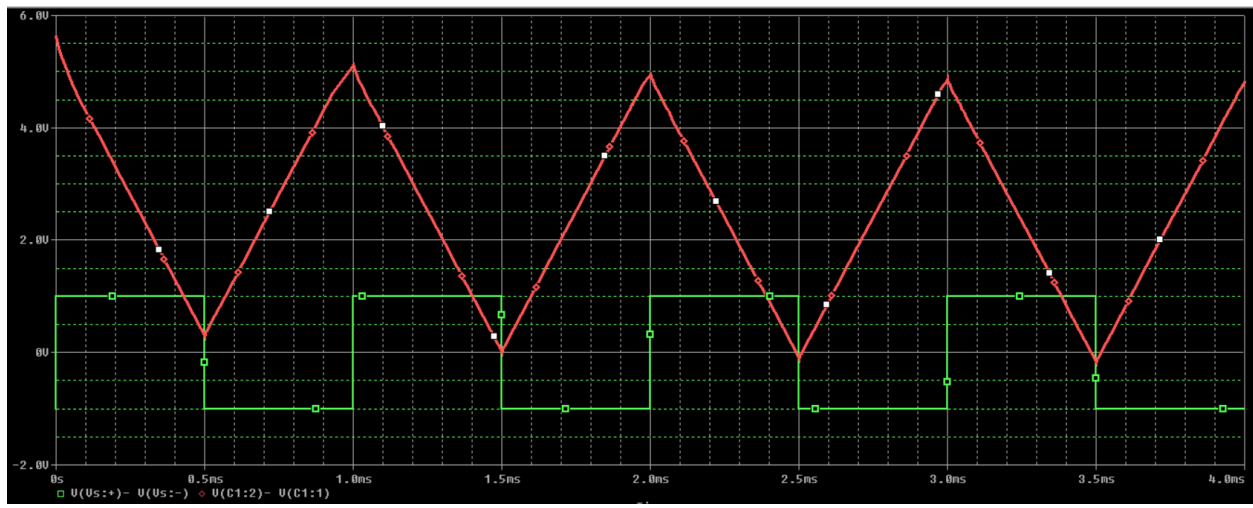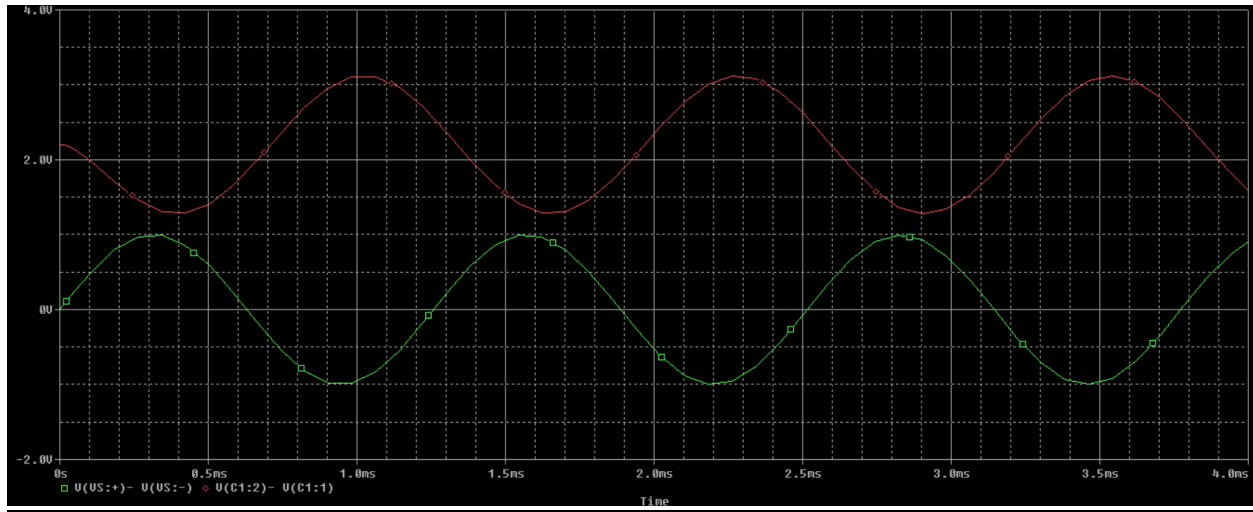

Conclusion:

We connect this circuit using Pspice software. I think if we could do this same experiment in the lab, the measure value would change a little bit and most importantly we could learn how to connect the circuit for real life.

