

A purba Roy

2018 3-60-063

MID-2




Apurba Roy

2018-B-60-063

Subject

Date: 1/1

Ans to the Q no 1

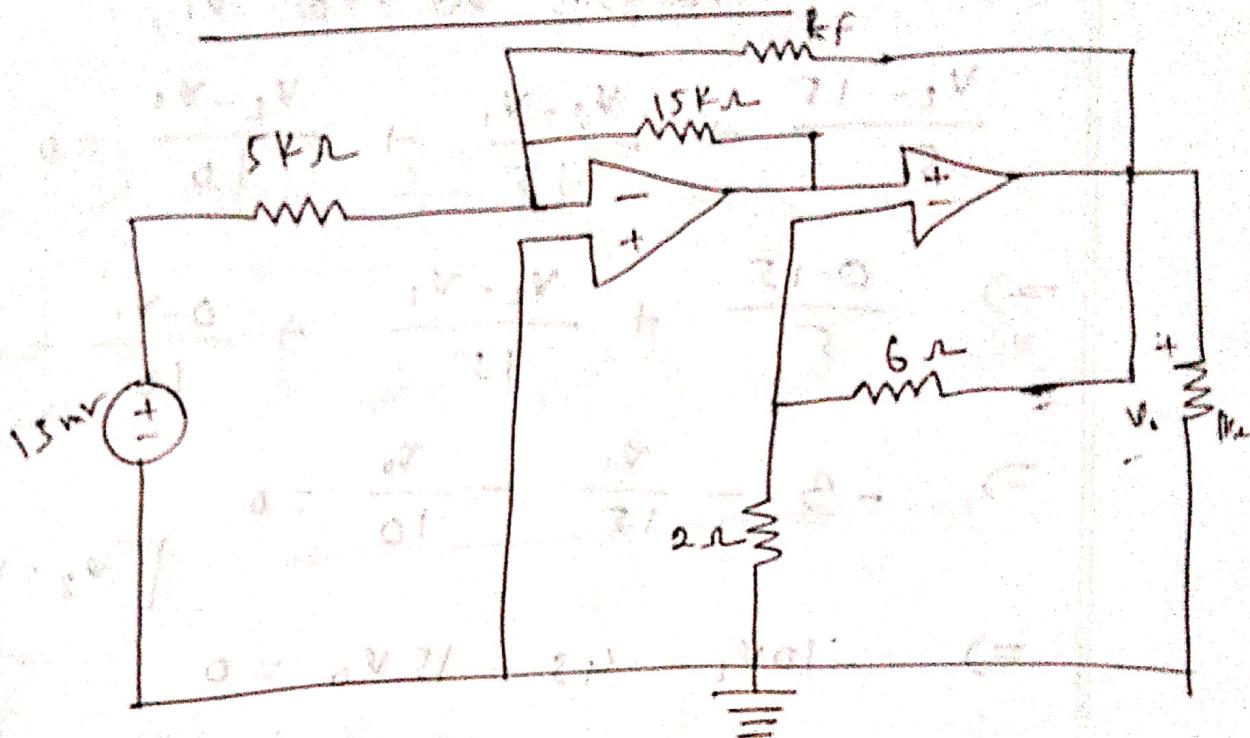

nodal analysis nod V_2 .

$$\frac{v_1}{2} + \frac{v_1 - v_0}{6} = 0$$

$$\Rightarrow \frac{v_1}{2} = -\frac{v_1 - v_0}{6}$$

$$\Rightarrow 6v_1 = -2v_1 + 2v_0$$

$$\Rightarrow 8v_1 = 2v_0$$

$$v_1 = \frac{v_0}{4}$$

nodal analysis at node V_1 ,

$$\frac{V_2 - 15}{5} + \frac{V_2 - V_1}{15} + \frac{V_2 - V_0}{10} = 0$$

$$\Rightarrow \frac{0 - 15}{5} + \frac{V_2 - V_1}{15} + \frac{0 - V_0}{10} = 0$$

$$\Rightarrow -3 - \frac{V_1}{15} - \frac{V_0}{10} = 0$$

$$\Rightarrow -10V_1 - 45 - 15V_0 = 0$$

$$\Rightarrow -10V_0 - 60V_0$$

$$\Rightarrow \frac{-70V_0}{9} = \frac{45}{9}$$

$$\Rightarrow V_0 = \frac{180}{70}$$

$$V_0 = -25\sqrt{3} \text{ mV}$$

Ans

Ans to the q no. 2

$$-V_{out} = \frac{V_1 - V_2}{3} + \frac{V_3}{2}$$

Soln :


$$-V_{out} = \frac{V_1 - V_2}{3} + \frac{V_3}{2}$$

$$\Rightarrow V_{out} = -\left(\frac{1}{3}V_1 - \frac{1}{3}V_2 + \frac{1}{2}V_3\right)$$


$$\Rightarrow V_{out} = -\left[\frac{1}{3}V_1 + \frac{1}{3}(-V_2) + \frac{1}{2}V_3\right]$$

$$\Rightarrow V_{out} = -\left[\frac{R}{3R}V_1 + \frac{R}{3R}\left(-\frac{R}{R}\right)V_2 + \frac{R}{2R}V_3\right]$$

The designed circuit is,

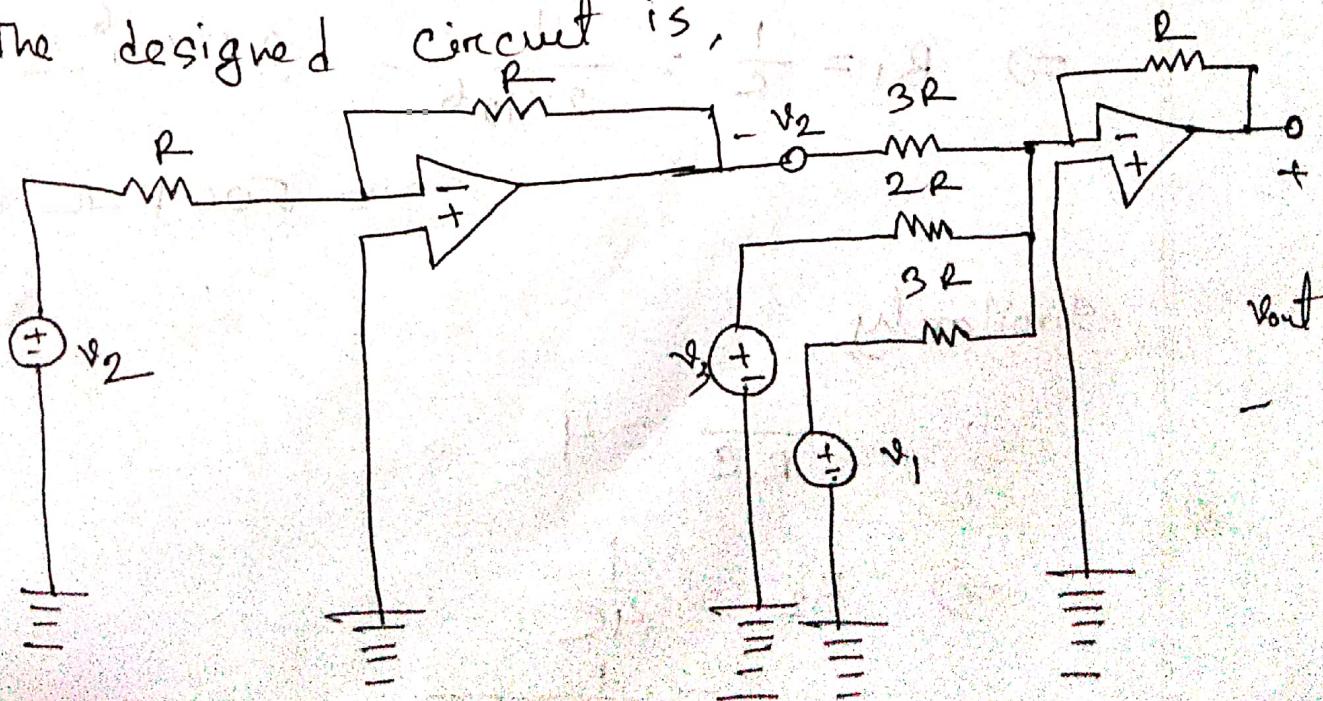

Ans to the q no. 3

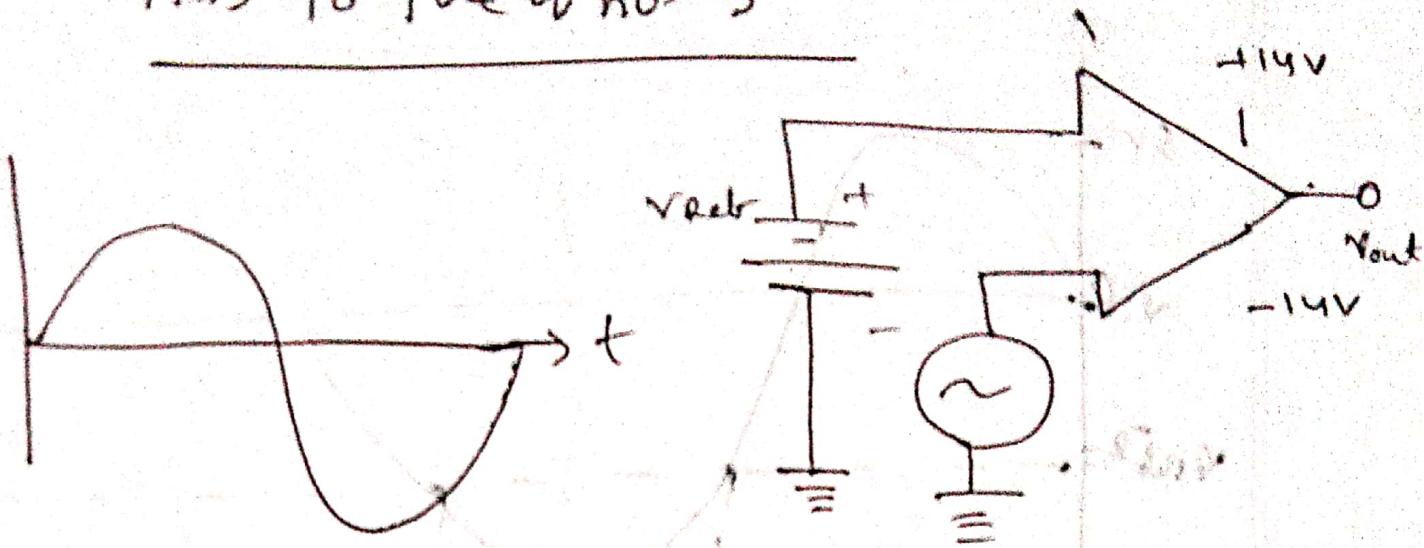

Here,

$$V_{ref} = -2V$$

When, $V_{in} > V_{ref}$, then. $V_o = +14V$


$V_{in} < V_{ref}$, then $V_o = -14V$

P.t.o

Date : / /

Subject :

Boi Bichitra

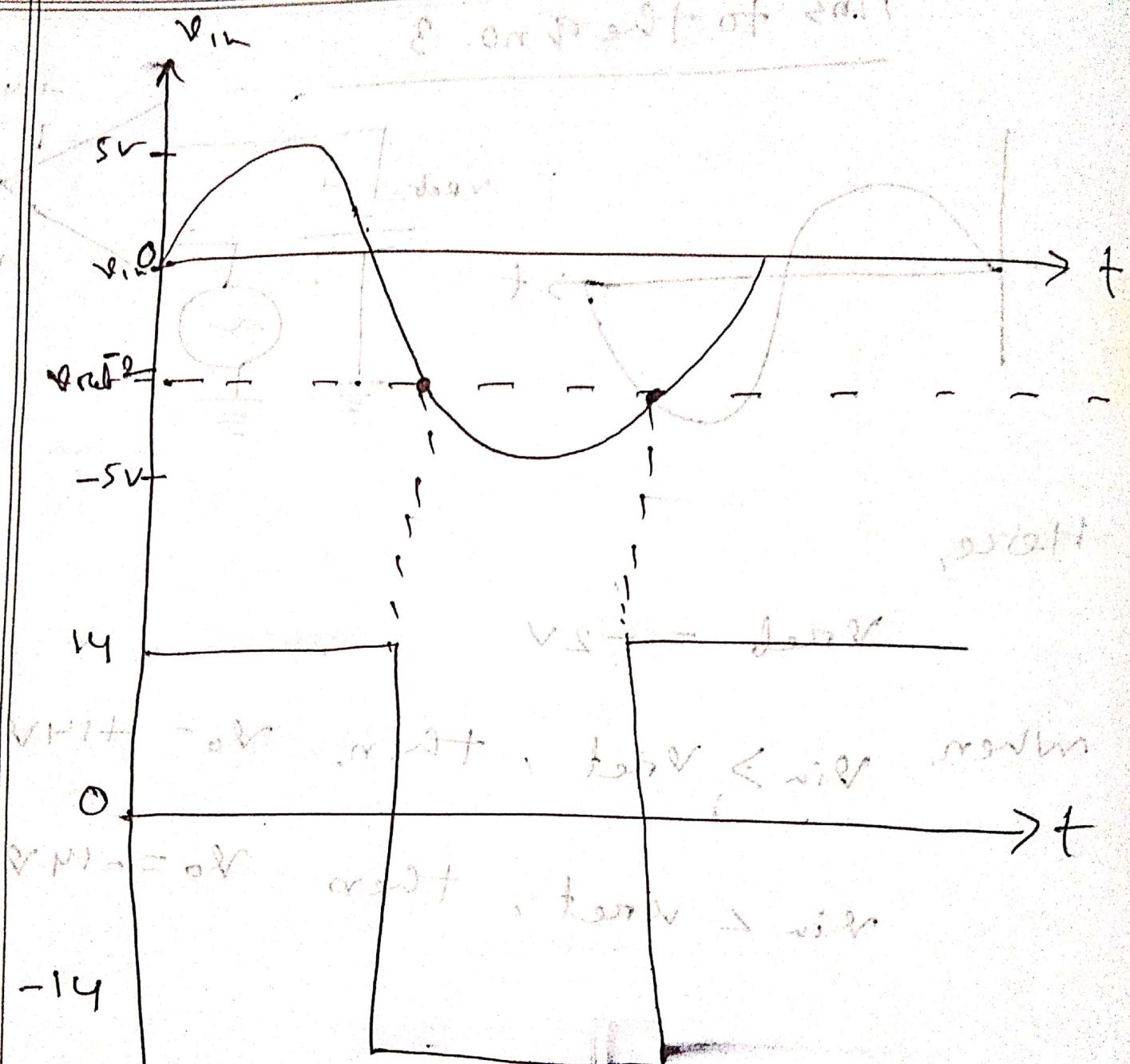

Subject:

Ans to the Q no - 4

Solⁿ: Using a single op amp the integrator circuit's output with three input signals

$$v_o = - \left[\frac{1}{R_1 C} \int v_1 dt + \frac{1}{R_2 C} \int v_2 dt + \frac{1}{R_3 C} \int v_3 dt \right] \quad (1)$$

Given,

$$v_o = - \int_0^t [v_1 + 4v_2 + 10v_3] dt \quad (ii)$$

Comparing (1) with (ii), we have,

$$\frac{1}{R_1 C} = 1$$

$$\Rightarrow R_1 = \frac{1}{C} = \frac{1}{2 \times 10^{-6}} = 0.5 \times 10^6 \Omega \\ = 500 \text{ k}\Omega$$

Similarly,

$$\frac{1}{R_2 C} = 4$$

$$\Rightarrow R_2 = \frac{1}{4C} \\ = \frac{1}{4 \times 2 \times 10^{-6}}$$

$$= 0.125 \times 10^6 \Omega$$

$$= 125 k\Omega$$

and,


$$\frac{1}{R_{3e}} = 10$$

(1) -



$$\Rightarrow R_3 = \frac{1}{10 \times 2 \times 10^{-6}} = 0.5 \times 10^5 \Omega$$

$$= 50 k\Omega$$

The designed circuit is, $2 \mu F$

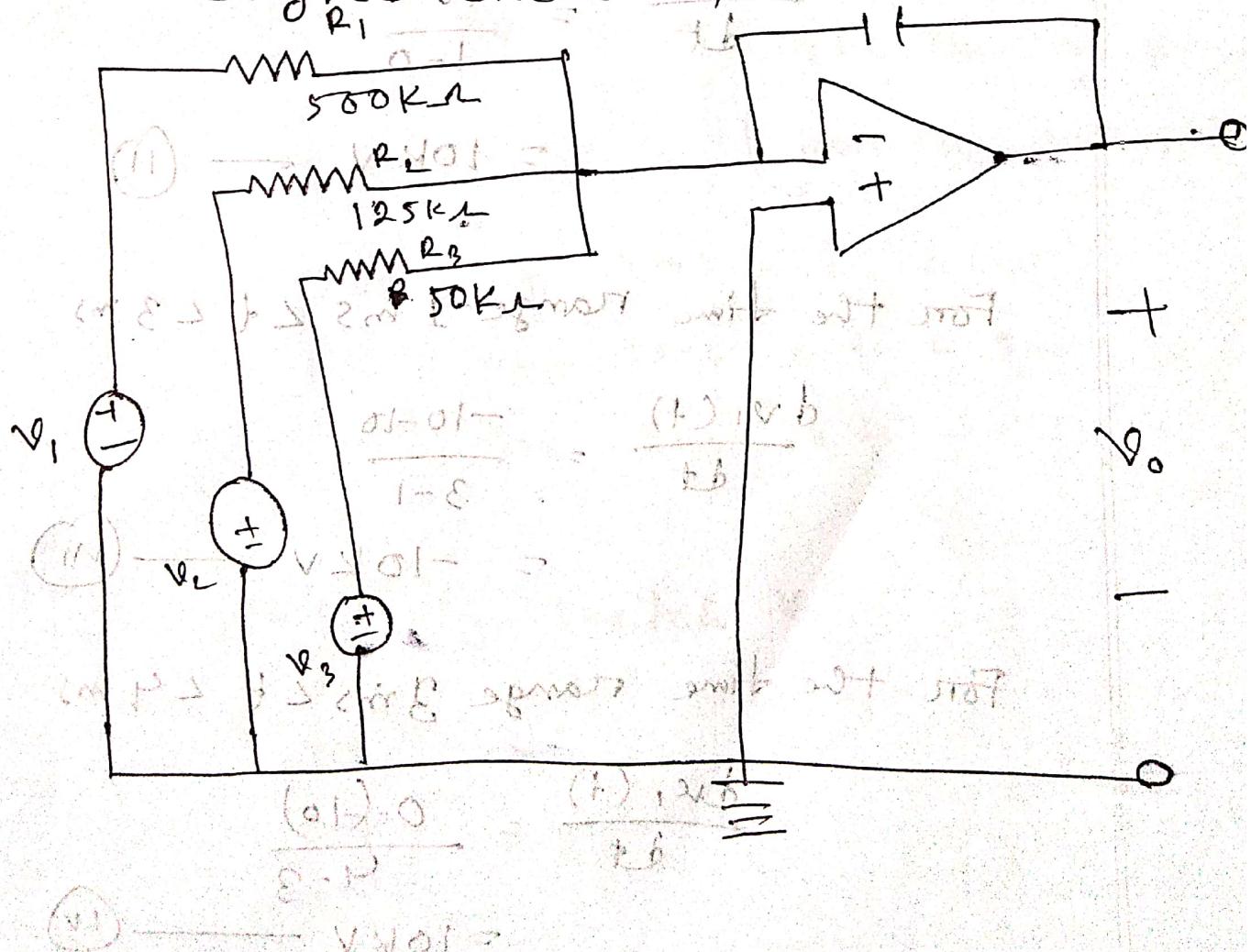

Ans to the Ques

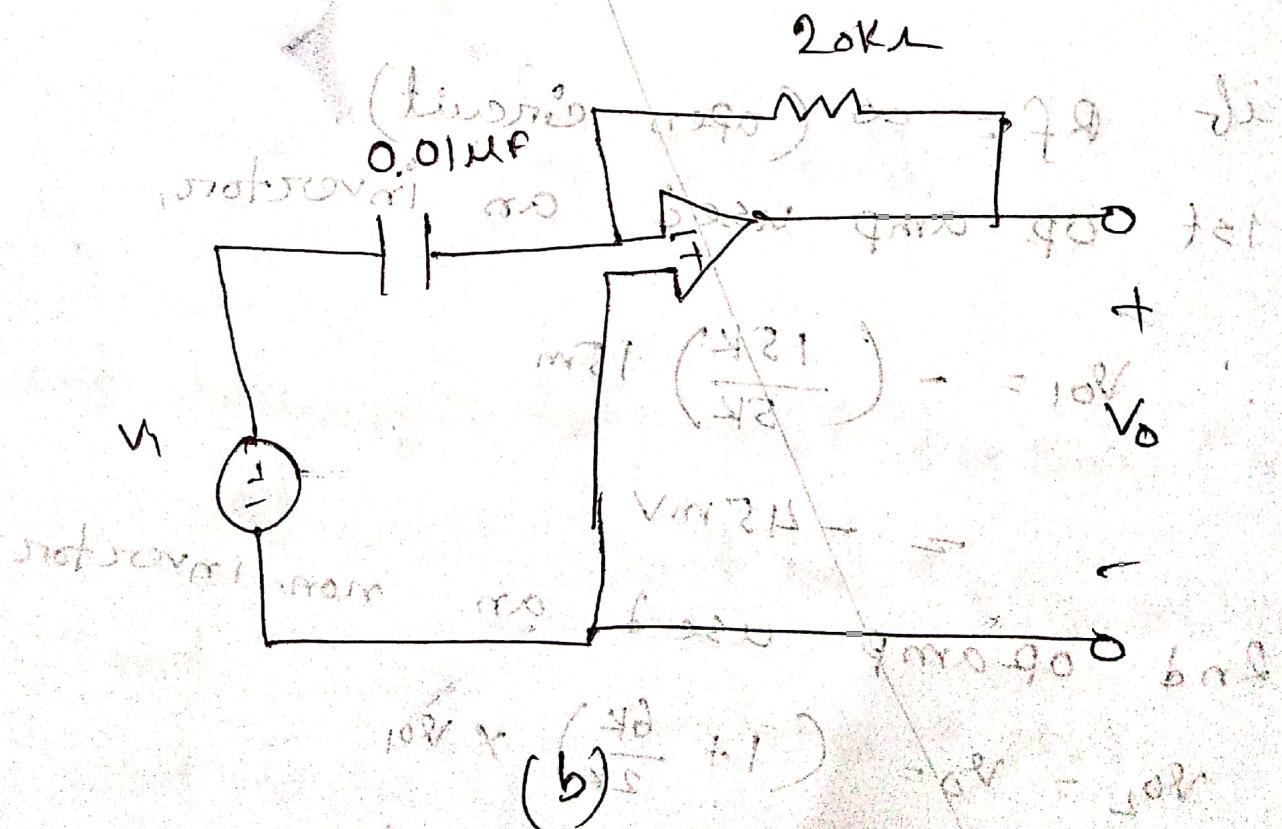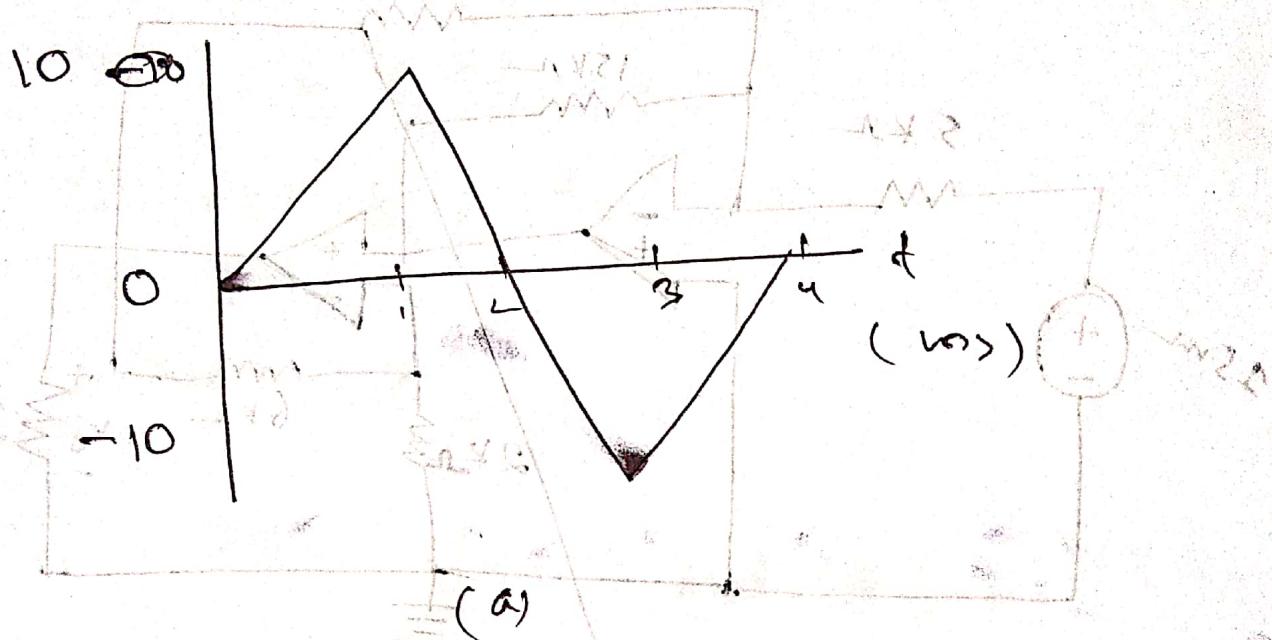

Subject :

~~Document No. 01X8X01~~

Solⁿ: The output voltage of the different


is given by,

$$V_o = -R_e \frac{dv_i(t)}{dt} \quad \text{--- (1)}$$

$$\Delta V_o = \frac{dV_i}{dt} = 8.9 \text{ V}$$

Then,

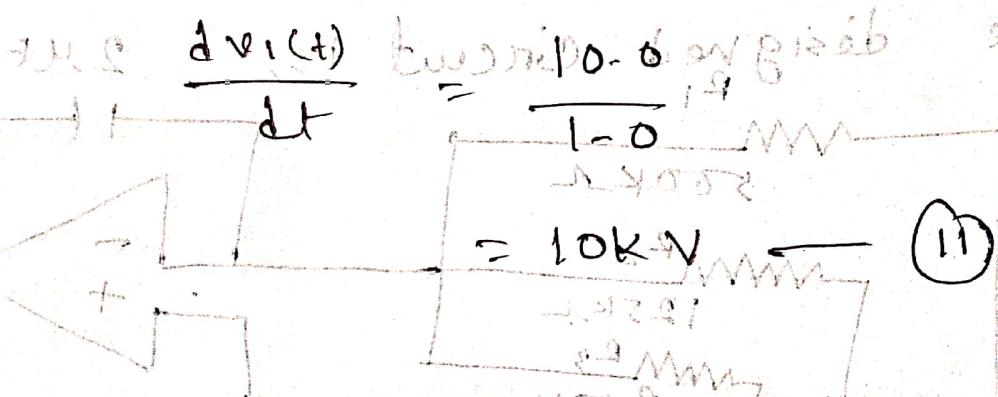For the time range $0 \text{ ms} < t < 1 \text{ ms}$



For the time range $1 \text{ ms} < t < 3 \text{ ms}$

$$\frac{dv_i(t)}{dt} = \frac{-10-10}{3-1} = -10 \text{ kV}$$

For the time range $3 \text{ ms} < t < 4 \text{ ms}$

$$\frac{dv_i(t)}{dt} = \frac{0-(-10)}{4-3} = 10 \text{ kV} \quad \text{--- (IV)}$$

From (i), (ii), (iii) and (iv),

$$\frac{dv_1(t)}{dt} = \begin{cases} 10\text{kV} & \text{for } 0\text{ms} \leq t < 1\text{ms} \\ -10\text{kV} & \text{for } 1\text{ms} \leq t < 3\text{ms} \\ 10\text{kV} & \text{for } 3\text{ms} \leq t < 4\text{ms} \end{cases}$$

(v)

Substitute with (v). When, $R = 20\text{k}\Omega$, $C = 0.01\mu\text{F}$

$$v_o(t) = -20 \times 10^3 \times 0.01 \times 10^{-6} \times \begin{cases} 10\text{kV} & \text{for } 0\text{ms} \leq t < 1\text{ms} \\ -10\text{kV} & \text{for } 1\text{ms} \leq t < 3\text{ms} \\ 10\text{kV} & \text{for } 3\text{ms} \leq t < 4\text{ms} \end{cases}$$

$$v_o(t) \rightarrow \begin{cases} -2\text{V} & \text{for } 0\text{ms} \leq t < 1\text{ms} \\ 2\text{V} & \text{for } 1\text{ms} \leq t < 3\text{ms} \\ -2\text{V} & \text{for } 3\text{ms} \leq t < 4\text{ms} \end{cases}$$

(vi)


Then, From (vi), sketch $v_o(t)$

Date : / /

Boi Bichitra

Subject :

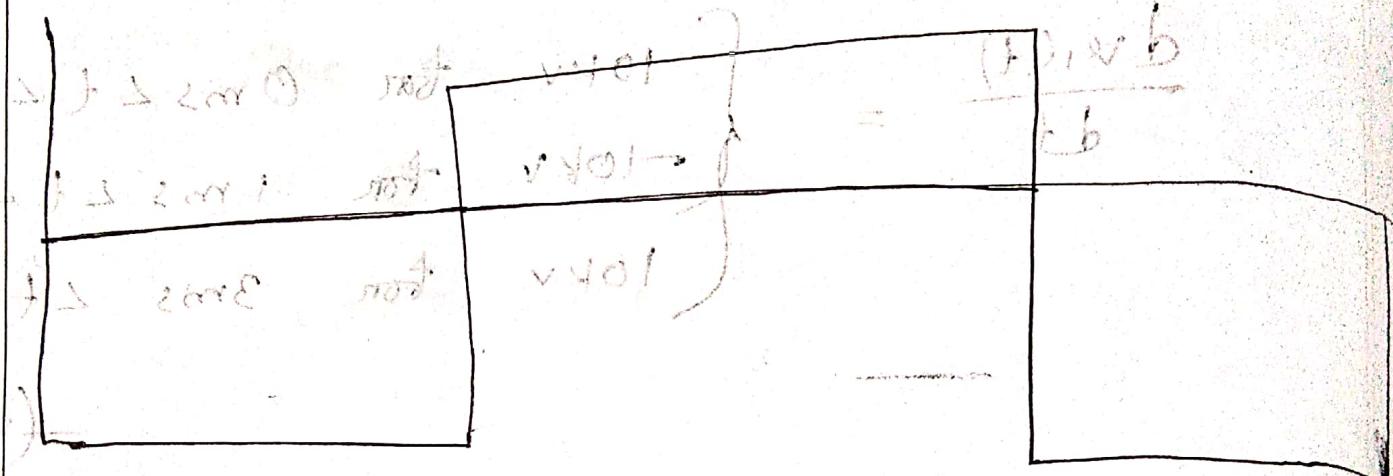(i) $\frac{dV}{dt}$ (ii) $\frac{dV}{dt} = 0$ (iii), (iv), (v)



0 0.5 1 1.5 2 2.5 3 3.5 4

2. $\frac{dV}{dt} > 0$ when $t < 1.5$ (i) $dV/dt = 0$ when $t = 1.5$

3. $\frac{dV}{dt} < 0$ when $t > 1.5$ (ii) $dV/dt = 0$ when $t = 1.5$

4. $\frac{dV}{dt} = 0$ when $t = 1.5$ (iii) $dV/dt > 0$ when $t < 1.5$

5. $\frac{dV}{dt} < 0$ when $t > 1.5$ (iv) $dV/dt = 0$ when $t = 1.5$


6. $\frac{dV}{dt} > 0$ when $t < 1.5$ (v) $dV/dt = 0$ when $t = 1.5$

7. $\frac{dV}{dt} < 0$ when $t > 1.5$ (vi) $dV/dt = 0$ when $t = 1.5$

8. $\frac{dV}{dt} > 0$ when $t < 1.5$ (vii) $dV/dt = 0$ when $t = 1.5$

(i) $dV/dt > 0$, (ii) $dV/dt = 0$

Ans to the q no 6.

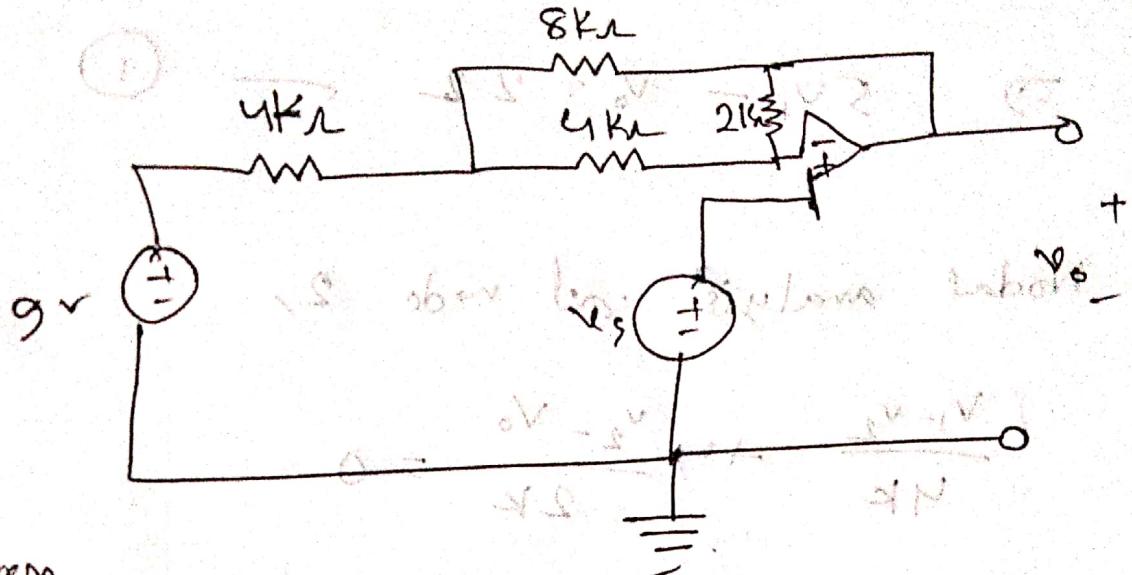

Given,

$$V_s = 2V \quad \theta = \frac{0V - 2V}{4k\Omega} = -\frac{2V}{4k\Omega}$$

$$\text{so, } V_s = V_2 = V_3 = 2V$$

At node 1 doing nodal analysis,

$$\frac{V_1 - V_{o1}}{8k\Omega} + \frac{V_1 - 9}{4k\Omega} + \frac{V_1 - V_2}{4k\Omega} = 0$$

$$\Rightarrow \frac{V_1 - V_o}{9k\Omega} + V_1 - 9 + V_1 - 2 = 0$$


$$\Rightarrow \frac{V_1 - V_o}{2k\Omega} + 2V_1 - 11 = 0$$

Subject :

Date :

Boi Bichitra
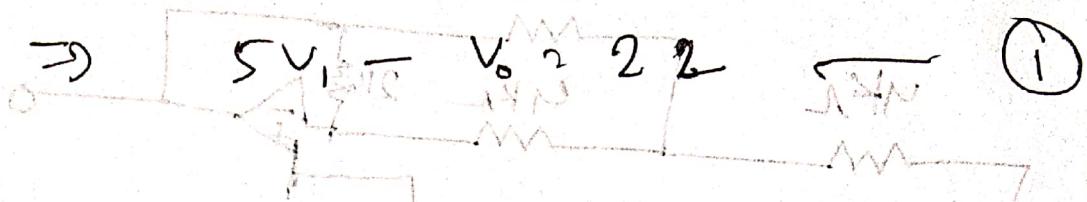
$$\Rightarrow \frac{V_1 - V_0 + 4V}{2k} = 11$$



Nodal analysis at node 2,

$$\frac{V_1 - V_2}{4k} + \frac{V_2 - V_0}{2k} = 0$$

$$\Rightarrow \frac{V_1 - 2}{4k} + \frac{2 - V_0}{2k} = 0$$

$$\Rightarrow V_1 - 2V_0 = 16$$

Combining equation (i) and (ii)

$$\Rightarrow V_0 = \sqrt{\frac{8}{11}}$$

So, closed-loop voltage gain

BB

Boi Bichitra

Subject :

Date : / /

Boi Bichitra

$$= \frac{V_0}{\sqrt{s}}$$

$$= \frac{8/11}{2}$$

$$\Rightarrow \frac{8}{11} \times \frac{1}{2}$$

$$= \frac{4}{11} V$$

$$= 0.3636 V$$

Ans.